

## Assignment Questions

- ① Derive the voltage gain, current gain, input impedance and output impedance of common Emitter using Small signal model.
- ② Derive the voltage gain, current gain, input impedance and output impedance of JFET common Drain Amplifier.
- ③ Derive the voltage gain, current gain, input impedance and output impedance of MOSFET common Source amplifier with unbypassed  $R_S$ .
- ④ Derive  $A_v$ ,  $A_i$ ,  $Z_i$ , &  $Z_o$  for common emitter amplifier with Emitter Resistor using small signal model.
- ⑤ What is a DC load line?
- ⑥ What is operating point?
- ⑦ List out advantages of  $h$ -Parameters?
- ⑧ How to obtain AC equivalent of a network?
- ⑨ Why CE Configuration is commonly used in applications?
- ⑩ Determine the operating point and draw DC load line and AC load line analysis of BJT and MOSFET.