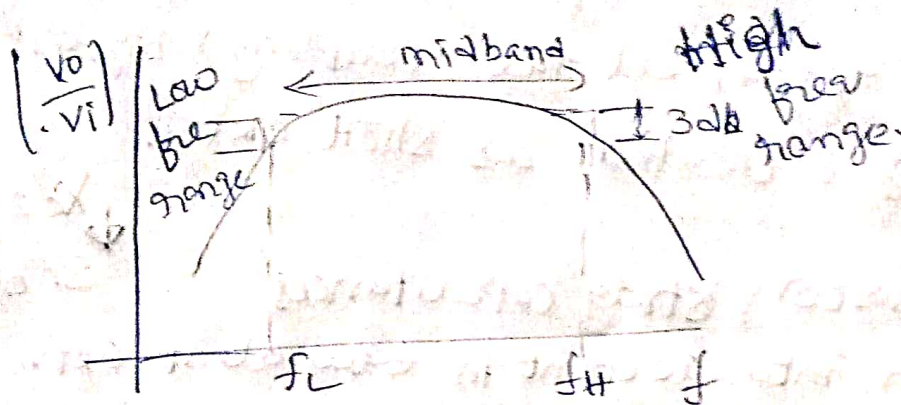


## unit - II

### Frequency response

All Amplifier gain factors are functions of signal frequency.  
→ These include voltage, current, transconductance and trans resistance.



The curve drawn between frequency & gain factor is called frequency response curve.

The frequency ranges are divided as:

- low frequency  $f < f_L$
- high frequency  $f > f_H$
- medium frequency.

$$20\text{Hz} < f < 20\text{kHz}$$

$$f_H > 20\text{kHz}$$

$$f_H$$

#### Frequency ranges

##### low frequency range

→ In this region, coupling and bypass capacitors must be included in the equivalent ckt and in the amplification factor calculations.

→ The stray and transition capacitances are treated as open ckt.

→ In low frequencies range,  $f < f_L$ , the gain ↓ as  $f$  ↓ because of coupling & bypass capacitor effects.




## High frequency range

- In this range all the stray & parasitic capacitances are present.
- due to these capacitances the gain decreases as frequency increase.
- In this range we use high frequency equivalent ckt.
- In this region all the coupling & bypass capacitors are going to be treated as short ckt.

$\downarrow X_{C2} \uparrow$   
 $\downarrow X_{C1} \uparrow$   
Short ckt.

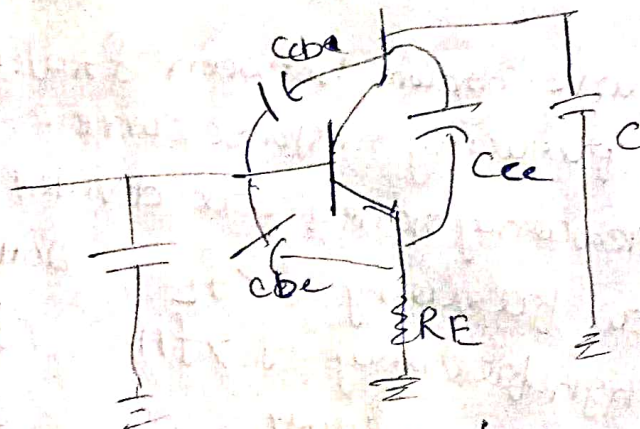- The transistor & stray capacitances are taken into account in equivalent ckt.




- due to p-n junction (between collector, base and emitter)
- $C_M$  &  $C_T$

## Midband Range :-

- coupling & bypass capacitors are treated as short ckt
- stray and transistor capacitances are treated as open ckt.
- so in this range no capacitors in the equivalent ckt.




short ckt and open ckt time constant

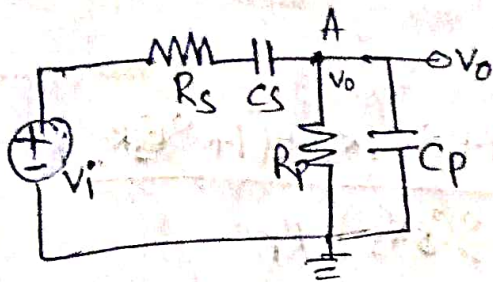

- $C_s$  is the coupling capacitor
- $C_p$  is the load capacitor and is in parallel with the output and ground.

- Applying KCL at output node

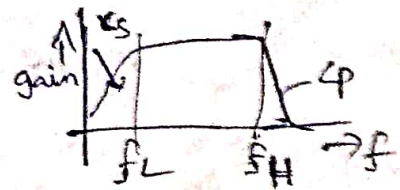

→ due to  $C_s$  at low frequencies the gain is going to be reduced

→ due to  $C_p$  at high frequencies the gain is going to be reduced. at mid freq the stray parasitic capacitances are appear so, gain maintains constant.

→ Applying

KCL at node A (ie) output node

$$\frac{V_o - V_i}{R_s + 1/sC_s} + \frac{V_o}{R_p} + \frac{V_o}{1/sC_p} = 0$$

$$\frac{(V_o - V_i) s C_s}{1 + s C_s R_s} + \frac{V_o}{R_p} + V_o \cdot s C_p = 0$$

separate  $V_o$  &  $V_i$  terms, to get the transfer function

$\frac{V_o}{V_i}$ . so, the equation becomes

$$V_o \left[ \frac{s C_s}{1 + s C_s R_s} + \frac{1}{R_p} + s C_p \right] = \frac{V_i s C_s}{1 + s C_s R_s}$$

$$\frac{V_o}{V_i} = \frac{s C_s}{1 + s C_s R_s \left[ \frac{s C_s}{1 + s C_s R_s} + \frac{1}{R_p} + s C_p \right]}$$



take LCM

$$\frac{V_o}{V_i} = \frac{S C_s}{1 + S C_s R_s \left[ \frac{S C_s R_p + 1 + S C_s R_s + (1 + S C_s R_s) R_p S C_p}{(1 + S C_s R_s) R_p} \right]}$$

$$\times = \frac{S C_s \cdot R_p}{1 + S C_s R_s \left[ \frac{1 + S C_s R_s}{R_p} \cdot \frac{C_p}{C_s} + R_p + R_s + \right]}$$

$$= \frac{S C_s R_p}{S C_s \left[ \frac{1}{S C_s} + R_s + R_p + (1 + S C_s R_s) R_p \frac{C_p}{C_s} \right]}$$

$$= \frac{R_p}{\left[ R_s + R_p + \frac{1}{S C_s} + (R_p + S C_s R_p R_s) \cdot \frac{C_p}{C_s} \right]}$$

$$= \left[ \frac{R_p}{R_s + R_p} \right] \left[ \frac{1}{1 + \frac{1}{S C_s (R_p + R_s)} + \left( \frac{R_p}{R_s + R_p} \right) \frac{C_p}{C_s} + \left( \frac{R_p R_s}{R_s + R_p} \right) \cdot S C_p} \right]$$

Series combination  
STs

parallel combination  
STp

$$\frac{V_{OC(S)}}{V_i(CS)} = \left[ \frac{R_p}{R_s + R_p} \right] \left[ \frac{1}{1 + \left( \frac{R_p}{R_s + R_p} \right) \frac{C_p}{C_s} + \frac{1}{S T_s} + S T_p} \right]$$





where

$$\tau_s = (R_s + R_p) C_s$$

$$\tau_p = \left( \frac{R_s R_p}{R_s + R_p} \right) C_p \quad \text{Time constants}$$

→

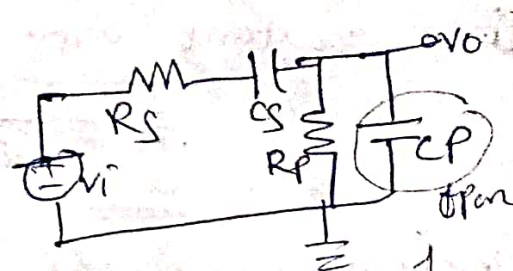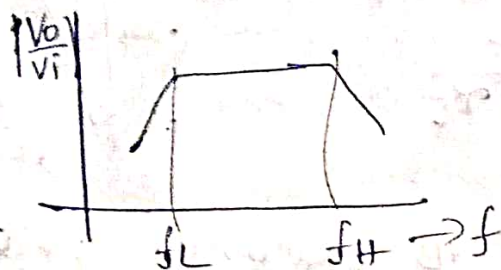

$C_s$  - affects the low frequency response


$C_p$  - affects the high frequency response

at low frequencies  $C_p$  as an open ckt  
if  $C_p \ll C_s$

To find the equivalent resistance seen by a capacitor, set all independent sources equal to zero.

∴ The effective resistance seen by  $C_s$  is the series combination of  $R_s$  &  $R_p$ .

The time constant of ckt is

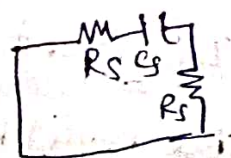

$$\tau_s = (R_s + R_p) C_s$$


Since  $C_p$  was made an open ckt,  $\tau_s$  is called an "open ckt" time constant.

⇒ At high frequencies,  $C_s$  coupling capacitor acts as a short ckt.



The effective resistance seen by  $C_p$  is the parallel combination of  $R_s$  and  $R_p$  and the associated time constant is
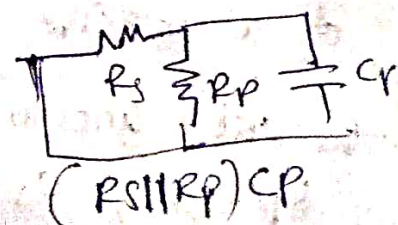
$$\tau_p = \left( \frac{R_s R_p}{R_s + R_p} \right) C_p$$



∴  $\tau_p$  is called the "short ckt" time constant.




Let consider

Side plot of the voltage transfer function magnitude

The lower corner (or) 3dB frequency, which is at the low end of the frequency scale, is a function of the circuit time constant and is defined as

$$f_L = \frac{1}{2\pi\tau_s}$$

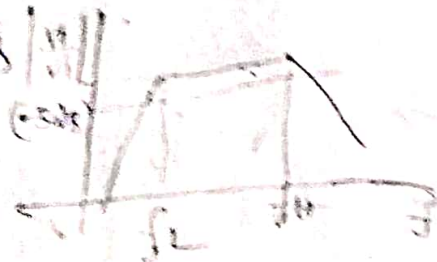

→ The upper corner (or) 3dB frequency which is at the high end of the frequency scale, is a function of the short circuit time constant and is defined as

$$f_H = \frac{1}{2\pi\tau_p}$$

→ The amplifier gain is constant over a wide frequency range, called the "midband".


→ In "midband" frequency range all capacitance effects are negligible (stray and parasitic capacitances)

→ The midband range (or) bandwidth is defined by the corner frequencies  $f_L$  and  $f_H$  as

$$BW = f_H - f_L$$

is:  $f_H \gg f_L$  then  $f_{BW} \approx f_H$
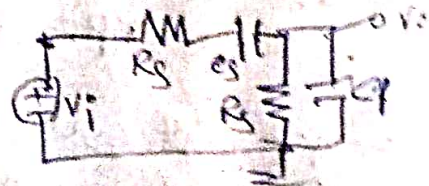
# Determine the corner frequencies and bandwidth of a passive ckt containing two capacitors, consider the ckt shown in figure, with parameters  $R_s = 1k\Omega$ ,  $R_p = 0k\Omega$ ,  $C_s = 1\mu F$  and  $C_p = 3pF$ .



sol:

$$\tau_s = (R_s + R_p) C_s = (10^3 + 10 \times 10^3)(10^{-6}) = 1.1 \times 10^{-2} \text{ s}$$

$$\tau_p = \left( \frac{R_s R_p}{R_s + R_p} \right) C_p = \frac{10^3 \times 10 \times 10^3}{10^3 + 10 \times 10^3} (3 \times 10^{-12}) = 2.73 \times 10^{-9} \text{ s}$$

$$f_L = \frac{1}{2\pi\tau_s} = \frac{1}{2\pi \times 1.1 \times 10^{-2}} = 14.5 \text{ Hz}$$

$$f_H = \frac{1}{2\pi\tau_p} = \frac{1}{2\pi (2.73 \times 10^{-9})} = 58.3 \text{ MHz}$$

$$f_{BW} = f_H - f_L = 58.3 \times 10^6 - 14.5 \text{ Hz} \approx 58.3 \text{ MHz} \quad \left[ \begin{matrix} f_H \gg f_L \\ BW \approx f_H \end{matrix} \right]$$


### Time Response :-

→ upto now, we observed steady state sinusoidal frequency response, we do for sinusoidal inputs.

→ In some cases, we may need to amplify other than sinusoidal signal also, i.e. pulse, square wave, triangular signals, i.e. digital signals.

→ In these cases, we need to consider the time response of output signals.

Consider ckt

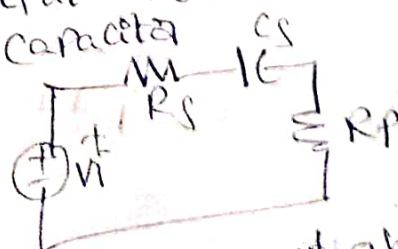

The voltage transfer function of above ckt

$$\begin{aligned} \frac{V_o(s)}{V_i(s)} &= \frac{R_p}{R_s + R_p + \frac{1}{sC_s}} \\ &= \frac{sC_s R_p}{1 + s(R_s + R_p)C_s} \end{aligned}$$




$$\frac{V_O(s)}{V_I(s)} = \left( \frac{R_P}{R_S + R_P} \right) \frac{S C R_S + R_P}{1 + S (R_S + R_P) C S}$$

$$\left( \frac{V_O}{V_I} \right) = K_2 \frac{S C}{1 + S T_2}$$

$$T_2 = (R_S + R_P) C S$$

$$K_2 = \frac{R_P}{R_S + R_P}$$

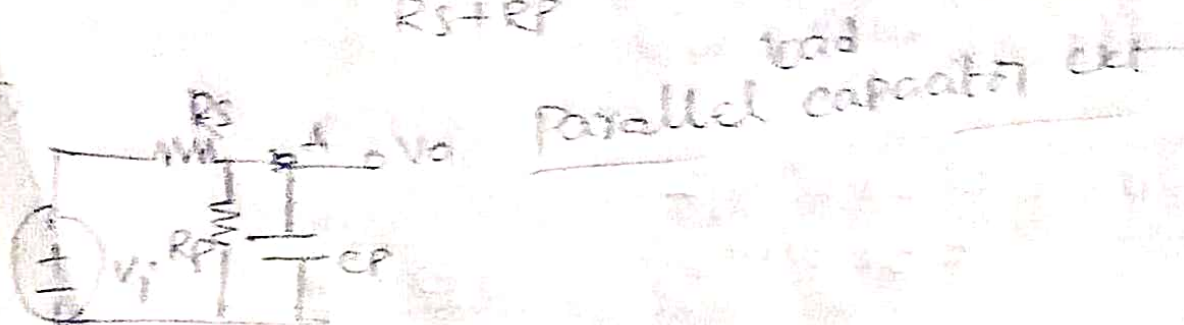

KCL at output node A

$$\frac{V_O - V_I}{R_S} + \frac{V_O}{R_P} + \frac{V_O}{1/s C P} = 0$$

$$\frac{V_O - V_I}{R_S} + \frac{V_O}{R_P} + \frac{V_O}{1/s C P} = \frac{V_I}{R_S}$$


$$\frac{V_O}{V_I} = \left( \frac{R_P}{R_S + R_P} \right) \frac{1}{1 + S \left( \frac{R_S R_P}{R_S + R_P} \right) C P}$$

$$= \left( \frac{R_P}{R_S + R_P} \right) \left( \frac{1}{S T_P + 1} \right)$$

$$T_P = (R_S \parallel R_P) C_P$$



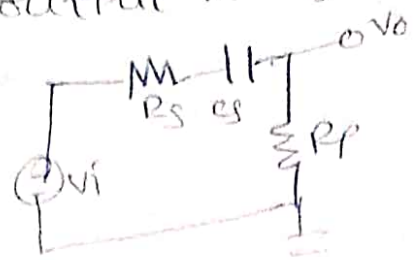In the input voltage is a step function  $V_i(s) = 1/s$ . <sup>(9) bc</sup>  
 series coupling capacitor ckt. Then output voltage <sup>can</sup>  
 $V_o(s) =$



$$V_o(s) = K_2 \left[ \frac{s\tau_2}{1 + s\tau_2} \right]$$

$$= \left( \frac{R_P}{R_S + R_P} \right) \left[ \frac{s(R_S + R_P) C_S}{1 + s(R_S + R_P) C_S} \right]$$

$$\frac{V_o(s)}{V_i(s)} = K_2 \left[ \frac{s\tau_2}{1 + s\tau_2} \right] \quad \text{if } V_i(s) = 1/s$$


$$= K_2 \left[ \frac{1}{s + 1/\tau_2} \right] \quad \frac{V_o(s)}{s} = K_2 \left[ \frac{\tau_2}{1 + s\tau_2} \right] \times \frac{1}{s}$$

$$= K_2 \left[ \frac{\tau_2}{1 + s\tau_2} \right]$$

$$= K_2 \left[ \frac{1}{s + 1/\tau_2} \right]$$

Taking inverse Laplace transformation, then

$$V_o(s) = K_2 e^{-t/\tau_2}$$

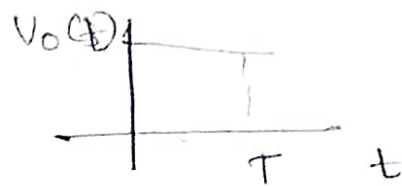


If we apply pulse input voltage, to above ckt the voltage applied to load ckt is slowly decreases.





In the input voltage is a step function  $V_i(s) = 1/s$ .  
Series coupling capacitor ckt. Then output voltage  $V_o(s) =$
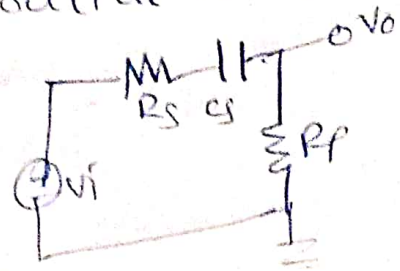
$$V_o(s) = K_2 \left[ \frac{s\tau_2}{1 + s\tau_2} \right]$$



$$= \left( \frac{R_p}{R_s + R_p} \right) \left[ \frac{s(R_s + R_p) C_s}{1 + s(R_s + R_p) C_s} \right]$$

$$\frac{V_o(s)}{V_i(s)} = K_2 \left[ \frac{s\tau_2}{1 + s\tau_2} \right] \quad \text{if } V_i(s) = 1/s$$


$$= K_2 \left[ \frac{1}{s + 1/\tau_2} \right] \quad \frac{V_o(s)}{V_i(s)} = K_2 \left[ \frac{s\tau_2}{1 + s\tau_2} \right] \times \frac{1}{s}$$

$$= K_2 \left[ \frac{\tau_2}{1 + s\tau_2} \right]$$

$$= K_2 \left[ \frac{1}{s + 1/\tau_2} \right]$$

Taking Inverse Laplace transformation, then

$$V_o(s) = K_2 e^{-t/\tau_2}$$

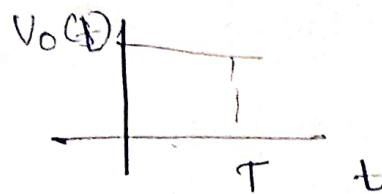

If we apply pulse input voltage, to above ckt the voltage applied to load ckt is slowly decreases.





we can rearrange the terms and write the function as

$$T(s) = K_1 \left( \frac{1}{1 + s\tau_1} \right) \quad (7.2(b))$$

where  $\tau_1$  is a time constant. Other transfer functions may be written as

$$T(s) = K_2 \left( \frac{s\tau_2}{1 + s\tau_2} \right) \quad (7.2(c))$$

where  $\tau_2$  is also a time constant. In most cases, we will write the transfer functions in terms of the time constants.

To introduce the frequency response analysis of transistor circuits, we will examine the circuits shown in Figures 7.2 and 7.3. The voltage transfer function for the circuit in Figure 7.2 can be expressed in a voltage divider format, as follows:

$$\frac{V_o(s)}{V_i(s)} = \frac{R_P}{R_S + R_P + \frac{1}{sC_S}} \quad (7.3)$$

The elements  $R_S$  and  $C_S$  are in series between the input and output signals, and the element  $R_P$  is in parallel with the output signal. Equation (7.3) can be written in the form

$$\frac{V_o(s)}{V_i(s)} = \frac{sR_P C_S}{1 + s(R_S + R_P)C_S} \quad (7.4)$$

which can be rearranged and written as

$$\frac{V_o(s)}{V_i(s)} = \left( \frac{R_P}{R_S + R_P} \right) \left[ \frac{s(R_S + R_P)C_S}{1 + s(R_S + R_P)C_S} \right] = K_2 \left( \frac{s\tau}{1 + s\tau} \right) \quad (7.5)$$

In this equation, the time constant is

$$\tau = (R_S + R_P)C_S$$

Writing a Kirchhoff current law (KCL) equation at the output node, we can determine the voltage transfer function for the circuit shown in Figure 7.3, as follows:

$$\frac{V_o - V_i}{R_S} + \frac{V_o}{R_P} + \frac{V_o}{(1/sC_P)} = 0 \quad (7.6)$$

In this case, the element  $R_S$  is in series between the input and output signals, and the elements  $R_P$  and  $C_P$  are in parallel with the output signal. Rearranging the terms in Equation (7.6) produces

$$\frac{V_o(s)}{V_i(s)} = \left( \frac{R_P}{R_S + R_P} \right) \left[ \frac{1}{1 + s \left( \frac{R_S R_P}{R_S + R_P} \right) C_P} \right] \quad (7.7)$$

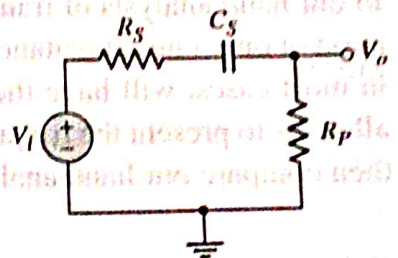


Figure 7.2 Series coupling capacitor circuit

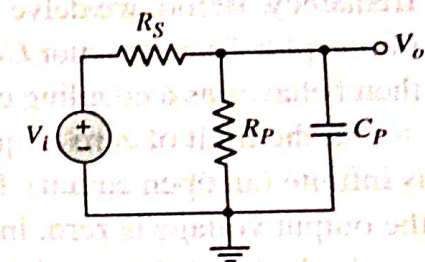


Figure 7.3 Parallel load capacitor circuit



or

$$\frac{V_o(s)}{V_i(s)} = \left( \frac{R_P}{R_S + R_P} \right) \left[ \frac{1}{1 + s(R_S \parallel R_P)C_P} \right] \quad (7.7(b))$$

In Equation (7.7(b)), the time constant is

$$\tau = (R_S \parallel R_P)C_P$$

## 7.2.2 First-Order Functions



of the pulse.

Consider, now, the circuit shown in Figure 7.18, which is a repeat of Figure 7.3. In this case, the capacitor  $C_P$  may represent the input capacitance of an amplifier. The transfer function was given in Equation (7.7(b)) as

$$\frac{V_o(s)}{V_i(s)} = \left( \frac{R_P}{R_S + R_P} \right) \cdot \left[ \frac{1}{1 + s(R_P \parallel R_S)C_P} \right] \quad (7.26)$$

or

$$\frac{V_o(s)}{V_i(s)} = K_1 \left( \frac{1}{1 + s\tau_1} \right) \quad (7.27)$$

where the time constant is  $\tau_1 = (R_P \parallel R_S)C_P$ .

Again, if the input signal is a step function, then  $V_i(s) = 1/s$ . The output voltage can then be written as

$$V_o(s) = \frac{K_1}{s} \left( \frac{1}{1 + s\tau_1} \right) = \frac{K_1}{s} \left( \frac{1/\tau_1}{s + 1/\tau_1} \right) \quad (7.28)$$

Taking the inverse Laplace transform, we find the output voltage time response as

$$v_o(t) = K_1(1 - e^{-t/\tau_1}) \quad (7.29)$$

If we are trying to amplify an input voltage pulse, we need to ensure that the time constant  $\tau_1$  is short compared to the pulse width  $T$ , so that the signal  $v_o(t)$  reaches a steady-state value. The output voltage is shown in Figure 7.19 for a square wave input signal. A short time constant implies a very small capacitor  $C_P$  as an input capacitance to an amplifier.

In this case, if the cutoff frequency of the transfer function is  $f_{3\text{-dB}} = 1/2\pi\tau_1 = 10$  MHz, then the time constant is  $\tau_1 = 15.9$  ns.

Figure 7.20 summarizes the steady-state output responses for square wave input signals of the two circuits we've just been considering. Figure 7.20(a) shows the steady-state output response of the circuit in Figure 7.16 (coupling capacitor) for a long time constant, and Figure 7.20(b) shows the steady-state output response of the circuit in Figure 7.18 (load capacitor) for a short time constant.

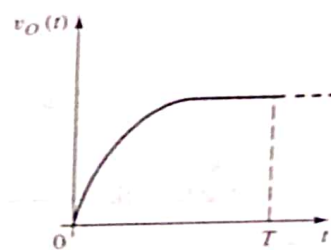


Figure 7.19 Output response of circuit in Figure 7.18 for a square-wave input signal and for a short time constant



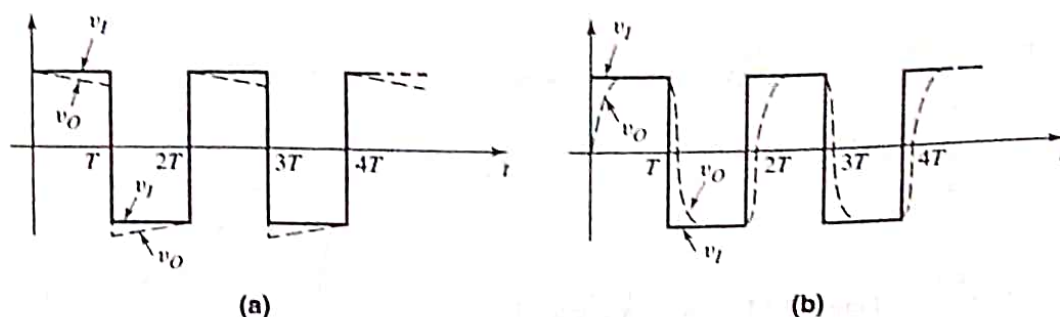


Figure 7.20 Steady-state output response for a square-wave input response for (a) circuit in Figure 7.16 (coupling capacitor) and a large time constant, and (b) circuit in Figure 7.18 (load capacitor) and a short time constant

### 7.3 FREQUENCY RESPONSE: TRANSISTOR AMPLIFIERS WITH CIRCUIT CAPACITORS

**Objective:** • Analyze the frequency response of transistor circuits with capacitors.

In this section, we will analyze the basic single-stage amplifier that includes circuit capacitors. Three types of capacitors will be considered: coupling capacitor, load capacitor, and bypass capacitor. In our hand analysis, we will consider each type of capacitor individually and determine its frequency response. In the last part of this section, we will consider the effect of multiple capacitors using a PSpice analysis.

The frequency response of multistage circuits will be considered in Chapter 12 when the stability of amplifiers is considered.

#### 7.3.1 Coupling Capacitor Effects

##### Input Coupling Capacitor: Common-Emitter Circuit

Figure 7.21(a) shows a bipolar common-emitter circuit with a coupling capacitor. Figure 7.21(b) shows the corresponding small-signal equivalent circuit, with the transistor small-signal output resistance  $r_o$  assumed to

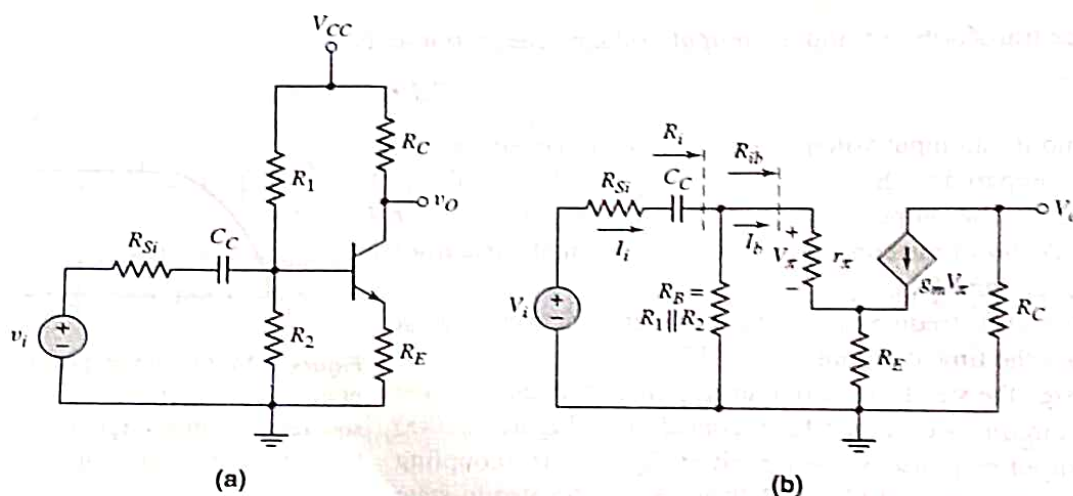


Figure 7.21 (a) Common-emitter circuit with coupling capacitor and (b) small-signal equivalent circuit

be infinite. This assumption is valid since  $r_o \gg R_C$  and  $r_o \gg R_E$  in most cases. Initially, we will use a current-voltage analysis to determine the frequency response of the circuit. Then, we will use the equivalent time constant technique.

From the analysis in the previous section, we note that this circuit is a high-pass network. At high frequencies, the capacitor  $C_C$  acts as a short circuit, and the input signal is coupled through the transistor to the output. At low frequencies, the impedance of  $C_C$  becomes large and the output approaches zero.

**Current-Voltage Analysis:** The input current can be written as

$$I_i = \frac{V_i}{R_{Si} + \frac{1}{sC_C} + R_i} \quad (7.30)$$

where the input resistance  $R_i$  is given by

$$R_i = R_B \parallel [r_\pi + (1 + \beta)R_E] = R_B \parallel R_{ib} \quad (7.31)$$

In writing Equation (7.31), we used the resistance reflection rule given in Chapter 6. To determine the input resistance to the base of the transistor, we multiplied the emitter resistance by the factor  $(1 + \beta)$ .

Using a current divider, we determine the base current to be

$$I_b = \left( \frac{R_B}{R_B + R_{ib}} \right) I_i \quad (7.32)$$

and then

$$V_\pi = I_b r_\pi \quad (7.33)$$

The output voltage is given by

$$V_o = -g_m V_\pi R_C \quad (7.34)$$

Combining Equations (7.30) through (7.34) produces

$$\begin{aligned} V_o &= -g_m R_C (I_b r_\pi) = -g_m r_\pi R_C \left( \frac{R_B}{R_B + R_{ib}} \right) I_i \\ &= -g_m r_\pi R_C \left( \frac{R_B}{R_B + R_{ib}} \right) \left( \frac{V_i}{R_{Si} + \frac{1}{sC_C} + R_i} \right) \end{aligned} \quad (7.35)$$

Therefore, the small-signal voltage gain is

$$A_v(s) = \frac{V_o(s)}{V_i(s)} = -g_m r_\pi R_C \left( \frac{R_B}{R_B + R_{ib}} \right) \left( \frac{sC_C}{1 + s(R_{Si} + R_i)C_C} \right) \quad (7.36)$$

which can be written in the form

$$A_v(s) = \frac{V_o(s)}{V_i(s)} = \frac{-g_m r_\pi R_C}{(R_{Si} + R_i)} \left( \frac{R_B}{R_B + R_{ib}} \right) \left( \frac{s\tau_S}{1 + s\tau_S} \right) \quad (7.37)$$

where the time constant is

$$\tau_S = (R_{Si} + R_i)C_C \quad (7.38)$$

The form of the voltage transfer function as given in Equation (7.37) is the same as that of Equation (7.5), for the coupling capacitor circuit in Figure 7.2. The Bode plot is therefore similar to that shown in Figure 7.5. The corner frequency is



$$f_L = \frac{1}{2\pi\tau_S} = \frac{1}{2\pi(R_{Si} + R_i)C_C} \quad (7.39)$$

and the maximum magnitude, in decibels, is

$$|A_v(\max)|_{dB} = 20 \log_{10} \left( \frac{g_m r_\pi R_C}{R_{Si} + R_i} \right) \left( \frac{R_B}{R_B + R_{ib}} \right) \quad (7.40)$$

### EXAMPLE 7.3

**Objective:** Calculate the corner frequency and maximum gain of a bipolar common-emitter circuit with a coupling capacitor.

For the circuit shown in Figure 7.21, the parameters are:  $R_1 = 51.2 \text{ k}\Omega$ ,  $R_2 = 9.6 \text{ k}\Omega$ ,  $R_C = 2 \text{ k}\Omega$ ,  $R_E = 0.4 \text{ k}\Omega$ ,  $R_{Si} = 0.1 \text{ k}\Omega$ ,  $C_C = 1 \text{ }\mu\text{F}$ , and  $V_{CC} = 10 \text{ V}$ . The transistor parameters are:  $V_{BE(\text{on})} = 0.7 \text{ V}$ ,  $\beta = 100$ , and  $V_A = \infty$ .

**Solution:** From a dc analysis, the quiescent collector current is  $I_{CQ} = 1.81 \text{ mA}$ . The transconductance is therefore

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1.81}{0.026} = 69.6 \text{ mA/V}$$

and the diffusion resistance is

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{1.81} = 1.44 \text{ k}\Omega$$

The input resistance is

$$\begin{aligned} R_i &= R_1 \parallel R_2 \parallel [r_\pi + (1 + \beta)R_E] \\ &= 51.2 \parallel 9.6 \parallel [1.44 + (101)(0.4)] = 6.77 \text{ k}\Omega \end{aligned}$$

and the time constant is therefore

$$\tau_S = (R_{Si} + R_i)C_C = (0.1 \times 10^3 + 6.77 \times 10^3)(1 \times 10^{-6}) = 6.87 \times 10^{-3} \text{ s}$$

or

$$\tau_S = 6.87 \text{ ms}$$

The corner frequency is

$$f_L = \frac{1}{2\pi\tau_S} = \frac{1}{2\pi(6.87 \times 10^{-3})} = 23.2 \text{ Hz}$$

Finally, the maximum voltage gain magnitude is

$$|A_v|_{\max} = \frac{g_m r_\pi R_C}{(R_{Si} + R_i)} \left( \frac{R_B}{R_B + R_{ib}} \right)$$

where

$$R_{ib} = r_\pi + (1 + \beta)R_E = 1.44 + (101)(0.4) = 41.8 \text{ k}\Omega$$

Therefore,

$$|A_v|_{\max} = \frac{(69.6)(1.44)(2)}{(0.1 + 6.775)} \left( \frac{8.084}{8.084 + 41.84} \right) = 4.72$$